 


Synchronous Counters

- A *synchronous counter*, in contrast to an *asynchronous counter*, is one whose output bits change state simultaneously, with no ripple.
- The only way we can build such a counter circuit from J-K flip-flops is to connect all the clock inputs together, so that each and every flip-flop receives the exact same clock pulse at the exact same time:



Example: General Circuit Diagram

How To Design Synchronous Counters

- For synchronous counters, all the flip-flops are using the same CLOCK signal. Thus, the output would change synchronously.
- Procedure to design synchronous counter are as follows:-
 - STEP 1:** Obtain the [State Diagram](#).
 - STEP 2:** Obtain the [Excitation Table](#) using state transition table for any particular FF (JK or D). Determine number of FF used.
 - STEP 3:** Obtain and simplify the function of each FF input using [K-Map](#).
 - STEP 4:** Draw the [circuit](#).

Synchronous Counters

Example 1: Design a MOD-4 Synchronous Up Counter, using JK FF.

STEP 1: Obtain the State transition Diagram



STEP 2: Obtain the Excitation table. Two JK FF are used.

OUTPUT TRANSITION			FF INPUT	
Q_N	$\rightarrow$	Q_{N+1}	J	K
0	$\rightarrow$	0	0	X
0	$\rightarrow$	1	1	X
1	$\rightarrow$	0	X	1
1	$\rightarrow$	1	X	0

Excitation table

Present State		Next State		Input, J K			
B	A	B	A	J_B	K_B	J_A	K_A
0	0	0	1	0	X	1	X
0	1	1	0	1	X	X	1
1	0	1	1	X	0	1	X
1	1	0	0	X	1	X	1

STEP 3: Obtain the simplified function using K-Map (Refer to input AB present state)

		B		
		0	1	
A	0	0	X	$J_B = A$
	1	1	X	


		B		
		0	1	
A	0	X	0	$K_B = A$
	1	X	1	

		B		
		0	1	
A	0	1	1	$J_A = 1$
	1	X	X	

		B		
		0	1	
A	0	X	X	$K_A = 1$
	1	1	1	

STEP 4: Draw the circuit diagram
 
$$J_B = A \quad K_B = A \quad J_A = 1 \quad K_A = 1$$




(MOD-4 Synchronous Up Counter)

Synchronous Counters

 Example 2: Design a Synchronous Counter to Count 4,7,3,0 and 2 respectively using JK Flip Flop negative triggered

STEP 1: Obtain the State transition Diagram



STEP 2: Obtain the Excitation table.

* Maximum Decimal Number is 7 = **1 1 1** in 3 bit binary, so 3 JK FF are used.

OUTPUT TRANSITION		FF INPUT	
Q_N	Q_{N+1}	J	K
0	→ 0	0	X
0	→ 1	1	X
1	→ 0	X	1
1	→ 1	X	0

Excitation table

Decimal	Present State			Next State			JC	KC	JB	KB	JA	KA
	QC	QB	QA	QC	QB	QA						
4	1	0	0	1	1	1	x	0	1	x	1	x
7	1	1	1	0	1	1	x	1	x	0	x	0
3	0	1	1	0	0	0	0	x	x	1	x	1
0	0	0	0	0	1	0	0	x	1	x	0	x
2	0	1	0	1	0	0	1	x	x	1	0	x

K-Map For

$$J_A = Q_C$$

	$\overline{CB}$	$\overline{C}B$	CB	$C\overline{B}$
$\overline{A}$	0	0	X	1
A	X	X	X	X

K-Map For

$$K_A = \overline{Q_C}$$

	$\overline{CB}$	$\overline{C}B$	CB	$C\overline{B}$
$\overline{A}$	X	X	X	X
A	X	1	0	X

STEP 3: Obtain the simplified function using K-Map (Refer to input AB present state)

K-Map For

$$J_B = 1$$

	$\overline{CB}$	$\overline{C}B$	CB	$C\overline{B}$
$\overline{A}$	1 4	X 5	X	1 1
A	X	X 3	X 2	X

K-Map For

$$K_B = \overline{Q_C}$$

	$\overline{CB}$	$\overline{C}B$	CB	$C\overline{B}$
$\overline{A}$	X	1	X	X
A	X	1	0	X

K-Map For

$$J_C = \overline{Q_A} \cdot Q_B$$

	$\overline{CB}$	$\overline{C}B$	CB	$C\overline{B}$
$\overline{A}$	0	1	X	X
A	X	0	X	X


K-Map For

$$K_C = Q_B$$

	$\overline{CB}$	$\overline{C}B$	CB	$C\overline{B}$
$\overline{A}$	X	X	X	0
A	X	X	1	X

STEP 4: Draw the circuit diagram
 
$$J_A = Q_C \quad K_A = \overline{Q_C} \quad J_B = 1 \quad K_B = \overline{Q_C} \quad J_C = \overline{Q_A} \cdot Q_B \quad K_C = Q_B$$



Exercise:

Design Counter to count the following sequence; $6 - 4 - 2 - 3 - 1$
Draw the Circuit Diagram.

Example: Design synchronous counter that counting from 0-1-3-7

* Maximum Decimal Number is 7 = **1 1 1** in 3 bit binary, so 3 JK FF are used.

OUTPUT TRANSITION		FF INPUT	
Q_N	Q_{N+1}	J	K
0	→ 0	0	X
0	→ 1	1	X
1	→ 0	X	1
1	→ 1	X	0

Excitation table

Decimal	Present State			Next State			JC	KC	JB	KB	JA	KA
	QC	QB	QA	QC	QB	QA						
0	0	0	0	0	0	1	0	X	0	X	1	X
1	0	0	1	0	1	1	0	X	1	X	X	0
3	0	1	1	1	1	1	1	X	X	0	X	0
7	1	1	1	0	0	0	X	1	X	1	X	1

Obtain the simplified function using K-Map (Refer to input AB present state)

K-Map For

$$J_A = 1$$

	$\overline{CB}$	$\overline{C}B$	CB	$C\overline{B}$
$\overline{A}$	1 1	X	X	X
A	2 X	3 X	4 X	X

K-Map For

$$K_A = Q_C$$

	$\overline{CB}$	$\overline{C}B$	CB	$C\overline{B}$
$\overline{A}$	X	X	X	X
A	0	0	1	X

K-Map For

$$J_B = Q_A$$

	$\overline{CB}$	$\overline{C}B$	CB	$C\overline{B}$
$\overline{A}$	0	X	X	X
A	1	X	X	X

K-Map For

$$K_B = Q_C$$

	$\overline{CB}$	$\overline{C}B$	CB	$C\overline{B}$
$\overline{A}$	X	X	X	X
A	X	0	1	X

K-Map For

$$J_C = Q_B$$

	$\overline{CB}$	$\overline{C}B$	CB	$C\overline{B}$
$\overline{A}$	0	X	X	X
A	0	1	X	X


K-Map For

$$K_C = 1$$

	$\overline{CB}$	$\overline{C}B$	CB	$C\overline{B}$
$\overline{A}$	X	X	X	X
A	X	X	1	X

Draw the circuit diagram
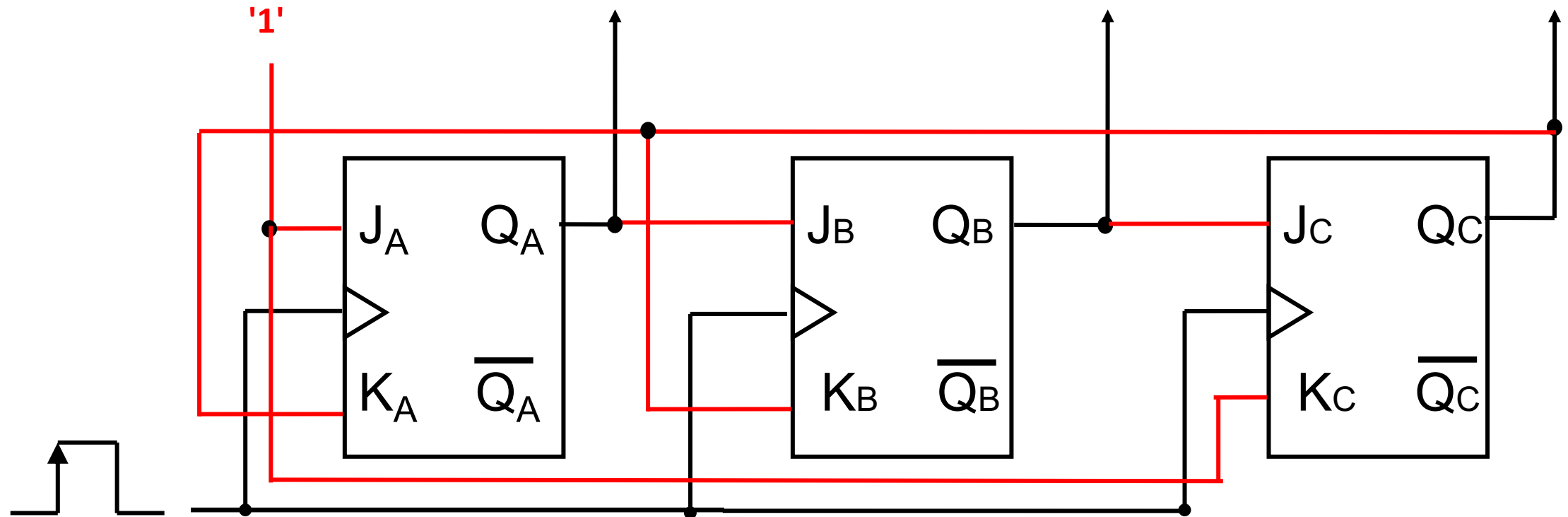
$$J_A = 1 \quad K_A = Q_C \quad J_B = Q_A \quad K_B = Q_C \quad J_C = Q_B \quad K_C = 1$$



Example: Design synchronous counter that counting from 0-1-3-4-5-7 using T Flip Flop

* Maximum Decimal Number is 7 = **1 1 1** in 3 bit binary, so 3 T Flip Flop are used.

OUTPUT TRANSITION		FF INPUT
Q_N	Q_{N+1}	T
0	→ 0	0
0	→ 1	1
1	→ 0	1
1	→ 1	0

Excitation table for T Flip Flop

Decimal	Present State			Next State			T_C	T_B	T_A
	Q_C	Q_B	Q_A	Q_C	Q_B	Q_A			
0	0	0	0	0	0	1	0	0	1
1	0	0	1	0	1	1	0	1	0
3	0	1	1	1	0	0	1	1	1
4	1	0	0	1	0	1	0	0	1
5	1	0	1	1	1	1	0	1	0
7	1	1	1	0	0	0	1	1	1

Obtain the simplified function using K-Map (Refer to input AB present state)

K-Map For

$$T_C = B = Q_B$$

	$\overline{B}A$	$\overline{B}\overline{A}$	BA	$B\overline{A}$
$\overline{C}$	0	0	1	X
C	0	0	1	X

K-Map For

$$T_B = A = Q_A$$

	$\overline{B}A$	$\overline{B}\overline{A}$	BA	$B\overline{A}$
$\overline{C}$	0	1	1	X
C	0	1	1	X

K-Map For

$$T_A = \overline{B} = \overline{Q_B}$$

	$\overline{B}A$	$\overline{B}\overline{A}$	BA	$B\overline{A}$
$\overline{C}$	1	1	0	X
C	1	1	0	X

Draw the circuit diagram

$$T_C = Q_B, T_B = Q_A, T_A = \overline{Q_B}$$

